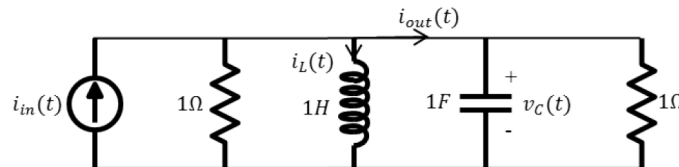


Set A

Consider the circuit shown below, where the excitation is $i_{in}(t) = 2 \sin(30t - 50^\circ) \text{ A}$. Assume that none of the elements carry energy at initial conditions.


- Find Thevenin's equivalent across the terminals of the rightmost 1Ω resistor (exclude the resistor while calculating Thevenin's equivalent).
- Using Thevenin's equivalent model, find the time domain current $i_{out}(t)$ and $v_C(t)$.



Set B

Consider the circuit shown below, where the excitation is $v_{in}(t) = 12 \sin(1t - 60^\circ) \text{ V}$. Assume that none of the elements carry energy at initial conditions.

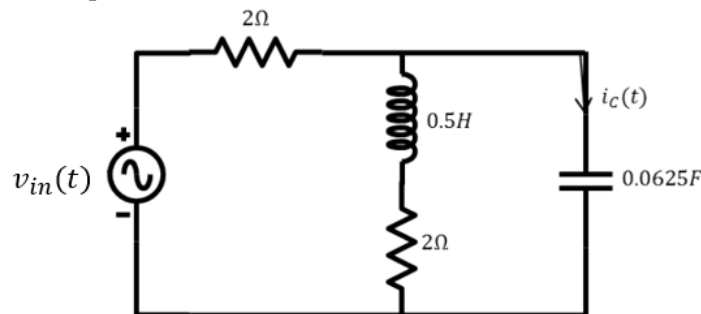
- Find Thevenin's equivalent across the terminals of the capacitor (exclude the capacitor while calculating Thevenin's equivalent).
- Using Thevenin's equivalent model, find the time domain current $i_C(t)$ passing through the capacitor and voltage $v_C(t)$ across the capacitor.



Set C

Consider the circuit shown below, where the excitation is $i_{in}(t) = 10 \cos(50t) \text{ A}$. Assume that none of the elements carry any energy at initial conditions.

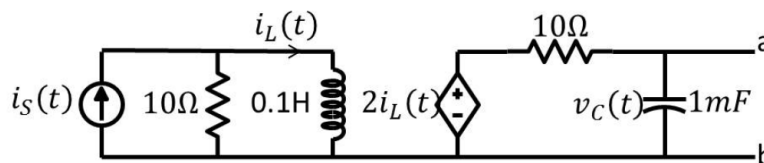
- Find Thevenin's equivalent across the terminals of the capacitor (exclude the capacitor while calculating Thevenin's equivalent).
- Using Thevenin's equivalent model, find the time domain current $i_L(t)$ and $v_C(t)$.



Set A

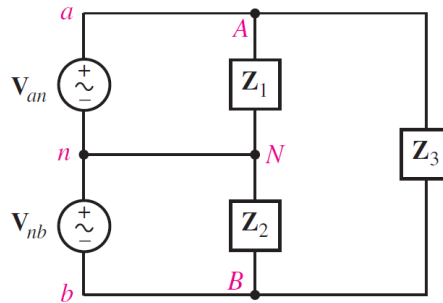Questions 1 [CO2]: Consider a single-phase three-wire system, as shown in the figure. The source is balanced and is operating at 60 Hz. \mathbf{V}_{an} is $110 + j0$ V rms. Assume the loads as $Z_1 = 50 + j0 \Omega$, $Z_2 = 100 + j45 \Omega$ and $Z_3 = 100 - j90 \Omega$. Write all answers with units.


- Find time-domain voltages $v_{an}(t)$ and $v_{bn}(t)$. Write your answers in terms of the cosine function with positive magnitude. [1]
- Find the instantaneous power delivered to each load. [5]
- Find the total average power supplied to loads. [2]
- Represent load Z_3 by a series combination of two passive elements. [2]



Set B

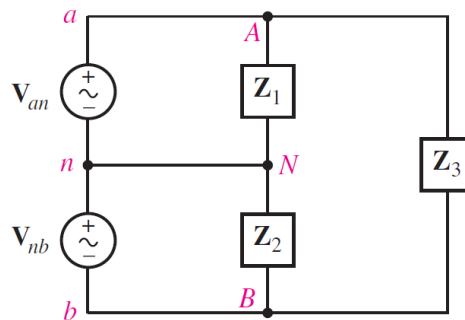Questions 1 [CO2]: Consider a single-phase three-wire system, as shown in the figure. The source is balanced and is operating at 60 Hz. \mathbf{V}_{an} is $110 + j0$ V rms. Assume the loads as $Z_1 = 50 + j0 \Omega$, $Z_2 = 100 + j45 \Omega$ and $Z_3 = 100 - j90 \Omega$. Write all answers with units.


- Find phasor currents I_{aA} and I_{bB} . [5]
- Find time-domain currents $i_{aA}(t)$ and $i_{bB}(t)$. [1]
- Find phasor current I_{nN} . [2]
- What would you change in the load to make I_{nN} equal to zero? Find the values of passive elements needed to implement this change. [2]



Set C

Questions 1 [CO2]: In the following figure, suppose the loads are $Z_1 = 100 + j0 \, \Omega$, $Z_2 = 200 + j90 \, \Omega$ and $Z_3 = 200 - j180 \, \Omega$. The balanced single-phase three-wire source operates at 50 Hz, and \mathbf{V}_{an} is $110 + j0 \, \text{V rms}$. Write all answers with units.

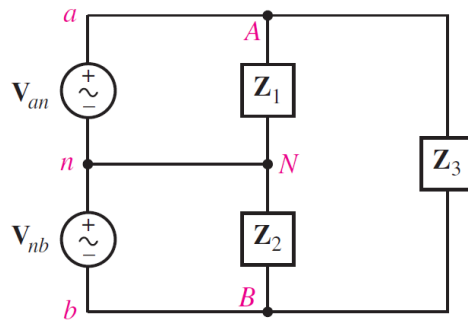
- (a) Find complex power delivered to each load. Write your answers in rectangular form. [5]
- (b) Find the average power delivered to each load. [1]
- (c) Find the total time-averaged power and total apparent power delivered by sources. [2]
- (d) Calculate the power factor of the total load and the power factor of the source. [2]



Set A

Questions 1 [CO2]: Consider the circuit represented in the figure. The coupling coefficient $k = 0.75$ and the source current $i_s = 5 \cos 200t$ mA.

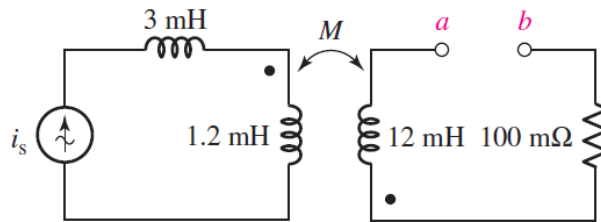- (a) Draw the circuit in the frequency domain. Specify all impedances in the circuit.
- (b) Calculate total energy stored at $t = 0$ if a-b is open-circuited.
- (c) Calculate total energy stored at $t = 0$ if a-b is short-circuited.



Set B

Questions 1 [CO2]: Consider the circuit represented in the figure.

- (a) Draw the circuit in the frequency domain. Specify all impedances in the circuit.
- (b) Obtain and simplify the mesh current equations.
- (c) Calculate the average power delivered to each resistor. [To help with calculations, the calculated value of the leftmost mesh current is provided as $0.74 \angle -73.2^\circ$ A.]

