

1. Consider the two inductances depicted

in fig. 1 Set $L_1 = 10\text{mH}$, $L_2 = 5\text{mH}$, and $M = 1\text{mH}$.

Determine the steady-state expression for (a) v_1 if $i_1 = 0$ and $i_2 = 5 \cos 8t \text{ A}$; (b) v_2 if $i_1 = 3 \sin 100t \text{ A}$ and $i_2 = 0$; (c) v_2 if $i_1 = 5 \cos(8t - 40^\circ) \text{ A}$ and $i_2 = 4 \sin 8t \text{ A}$.

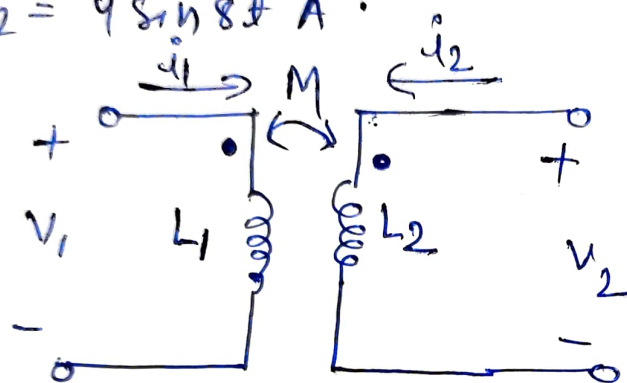


fig 1

2. For the circuit of fig: 2 (a) draw the phasor representation; (b) write a complete set of mesh equations; (c) calculate i_2 if $v_1(t) = 8 \sin 720t \text{ V}$.

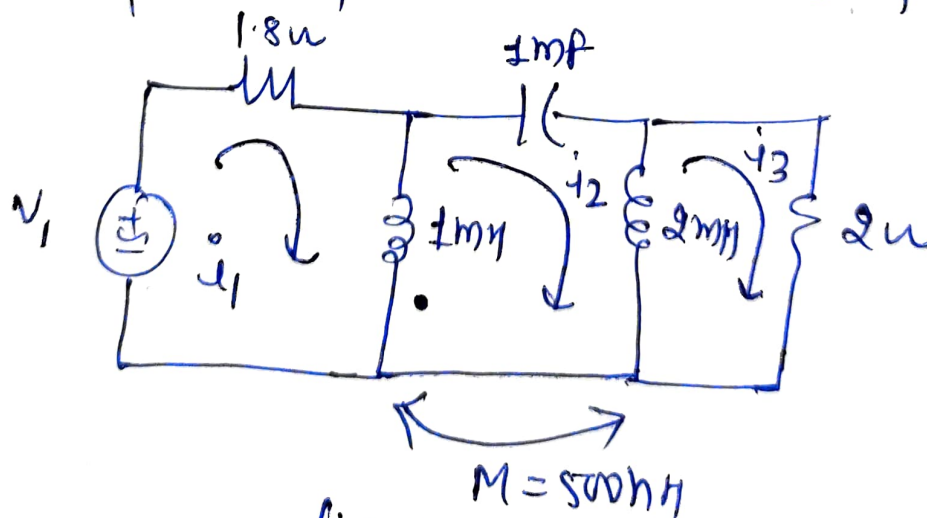


fig 2

3. Note that there is no mutual coupling between the $5H$ and $6H$ inductors in the circuit of fig 3.

(a) Write a set of equations in terms of $I_1(j\omega)$, $I_2(j\omega)$, and $I_3(j\omega)$.

(b) Find $I_3(j\omega)$, if $\omega = 2 \text{ rad/s}$.

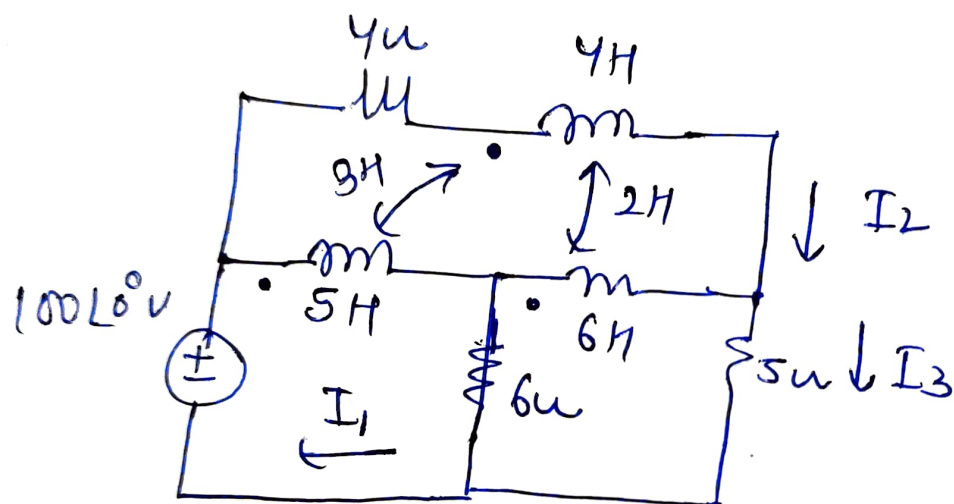


fig:3

4. Assume the following values for the circuit depicted schematically in fig 4.

$R_1 = R_2 = 5\Omega$, $L_1 = 24H$, $L_2 = 14H$ and $M = 80mH$.

Calculate the input impedance for $\omega = 10^7 \text{ rad/s}$. if Z_L is equal to

(a) 1Ω , (b) $j\Omega$ (c) $-j\Omega$ (d) $5\angle 33^\circ \Omega$.

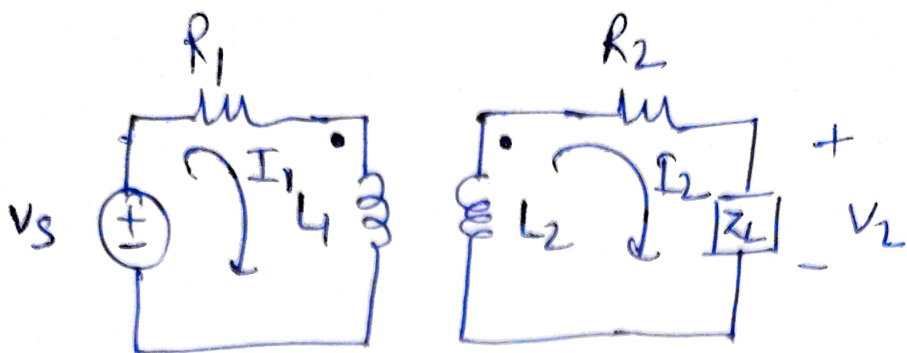


fig 4.

Q-5 (a) for the circuit of fig 5, if $V_s = 8 \cos 1000t$ V, calculate V_o .

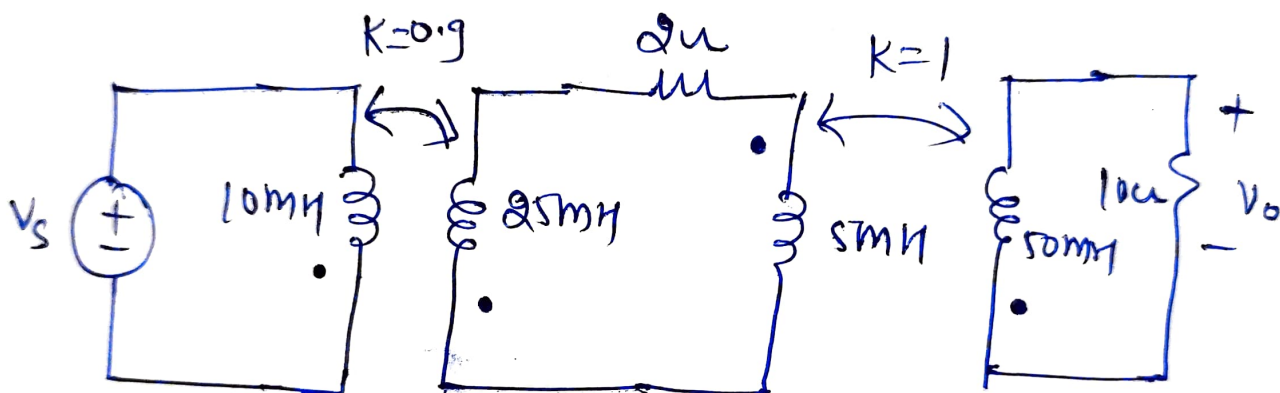


fig 5