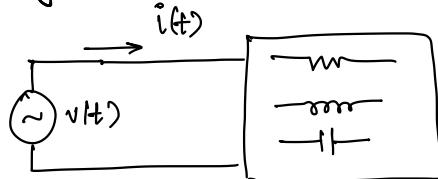


Module 3

AC Power Analysis



$$\cos A \cdot \cos B = \frac{1}{2} [\cos(A+B) + \cos(A-B)]$$

Instantaneous Power : $p(t) = v(t) i(t)$

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$


$$p(t) = V_m \cos(\omega t + \theta) \cdot I_m \cos(\omega t + \phi)$$

$$= \underbrace{\frac{V_m I_m}{2} \cos(\theta - \phi)}_{\text{constant}} + \underbrace{\frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi)}_{\text{twice frequency (harmonic)}}$$

Average Power :

$$\begin{aligned} P_{avg} &= \frac{1}{T} \int_0^T p(t) dt \\ &= \underbrace{\frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(\theta - \phi) dt}_{\text{constant}} + \underbrace{\frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(2\omega t + \theta + \phi) dt}_{0} \\ &= \frac{V_m I_m}{2} \cos(\theta - \phi) + 0 \end{aligned}$$

Average of \cos

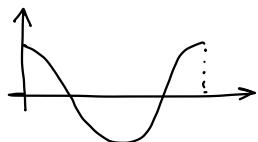

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi)$$

$$P_{avg} = \frac{1}{2} \operatorname{Re} \{ \mathbf{V} \mathbf{I}^* \}$$

$$\mathbf{I} = I_m e^{j\phi}$$

$$\mathbf{I}^* = I_m e^{-j\phi}$$


~~$P_{avg} = \mathbf{V} \mathbf{I}^*$~~

No phasor for power!

Average power absorbed by a
purely resistive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\Theta - \phi)$$

\uparrow \uparrow

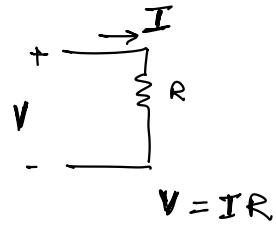


$$P_{avg} = \frac{V_m I_m}{2} = \frac{I_m^2 R}{2} = \frac{V_m^2}{2R}$$

Purely inductive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\Theta - \phi)$$

$$= \frac{V_m I_m}{2} \cos(90^\circ)$$

$$\boxed{P_{avg} = 0}$$

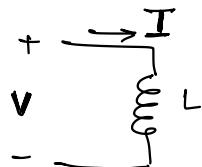

$$\mathbf{V} = j\omega L \mathbf{I}$$

$$(\Theta - \phi) =$$

$$\Rightarrow V_m e^{j\Theta} = j\omega L I_m e^{j\phi}$$

$$\Rightarrow \underbrace{\frac{V_m}{I_m}}_{e^{j\Theta-\phi}} = j\omega L \quad \Theta - \phi = 90^\circ$$

Purely capacitive element

$$P_{avg} = \frac{V_m I_m}{2} \cos(\Theta - \phi)$$

$$\Theta - \phi = -90^\circ$$

$$\boxed{P_{avg} = 0}$$

$p(t)$

$$P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi) \quad \checkmark$$

$$P_{avg} = \operatorname{Re} \left\{ \frac{V I^*}{2} \right\}$$


$$v(t) = V_m \cos(\omega t + \theta)$$

$$v(t) = \operatorname{Re} \left\{ V_m e^{j\omega t + j\theta} \right\}$$


$$e^{j\omega t}$$

$$V = V_m \angle \theta$$

Example

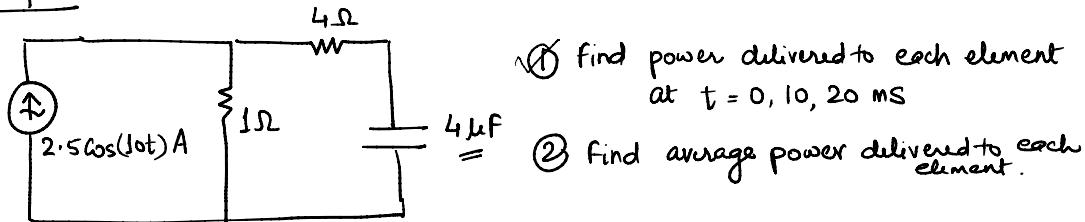

In frequency domain

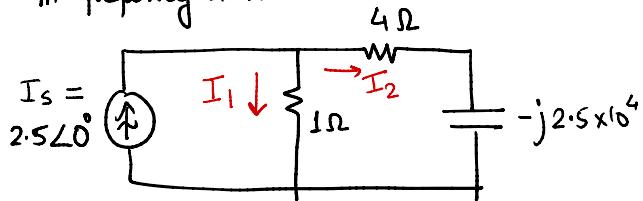

Power delivered to 1Ω

$$P_{1\Omega}(t) = V_{1\Omega}(t) i_p(t)$$

$$I_{1\Omega} = I_1 = I_s \frac{\frac{4-j2.5 \times 10^4}{1+4-j2.5 \times 10^4}}{\approx I_s \Rightarrow i_{1\Omega}(t) = 2.5 \cos(10t) A}$$

$$V_{1\Omega} = (I_1)(1\Omega) \Rightarrow V_{1\Omega}(t) = 2.5 \cos(10t) V$$

$$P_{1\Omega}(t) = 2.5 \cos(10t) \cdot 2.5 \cos(10t)$$

$$P_{1\Omega}(t) = 3.125 + 3.125 \cos(20t) \text{ Watts}$$

$$P_{1\Omega}(t=0) = 6.25 \text{ W}$$

$$P_{1\Omega}(t=10\text{ms}) = 6.1877 \text{ W}$$

$$P_{1\Omega}(t=20\text{ms}) = 6.0033 \text{ W}$$

Average power delivered to 1Ω

$$P_{avg, 1\Omega} = 3.125 \text{ W}$$

Power delivered to 4Ω :-

$$P_{4\Omega}(t) = V_{4\Omega}(t) \cdot i_{4\Omega}(t)$$

$$I_{4\Omega} = I_2 = I_s \frac{1}{S - j 2.5 \times 10^4} = 10^4 \angle 90^\circ A \rightarrow i_{4\Omega}(t)$$

$$V_{4\Omega} = 4(I_{4\Omega}) = 4 \times 10^4 \angle 90^\circ V \rightarrow v_{4\Omega}(t)$$

$$P_{4\Omega}(t) = 2 \times 10^{-8} + 2 \times 10^{-8} \cos(20t) W$$

$$P_{4\Omega}(t=0) = 4 \times 10^{-8} W$$

$$P_{4\Omega}(t=10ms) = 3.96 \times 10^{-8} W$$

$$P_{4\Omega}(t=20ms) = 3.84 \times 10^{-8} W$$

$$P_{avg, 4\Omega} = 2 \times 10^{-8} W$$

Power delivered to capacitor :-

$$P_C(t) =$$

$$P_{avg, C} =$$

$$I_c = I_2 = 10^4 \angle 90^\circ A \leftarrow \rightarrow i_c(t) \Rightarrow p(t) = i_c(t)v_c(t) \checkmark$$

$$V_c = (j 2.5 \times 10^4) I_2 = 2.5 V \rightarrow v_c(t)$$

$$\underbrace{i_c \times v_c}_{\text{Phasor of power}} \rightarrow p(t)$$

$$i_c(t) = 10^4 \cos(10t + 90^\circ)$$

$$v_c(t) = 2.5 \cos(10t)$$

$$P_C(t) = 1.25 \times 10^{-4} \cos(20t + 90^\circ) W$$



$$P_C(t=0) = 0 W$$

$$P_C(t=10ms) = 2.48 \times 10^{-5} W$$

$$P_C(t=20ms) = 4.86 \times 10^{-5} W$$


$$P_{avg, C} = 0$$

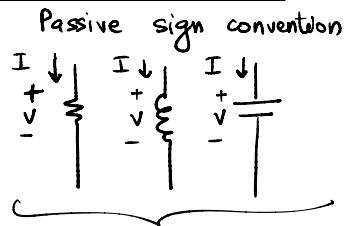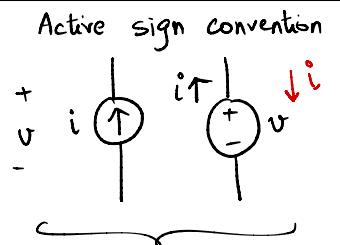- ① $P_{1\Omega}(t) + P_{4\Omega}(t) + P_C(t) = \text{constant 1}$ X
- ② $P_{\text{avg}, 1\Omega} + P_{\text{avg}, 4\Omega} + P_{\text{avg}, C} = \text{constant 2}$ \checkmark $= P_{\text{avg, source}}$



$$v \cdot i = -20 \text{ W}$$



Maximum Power Transfer :

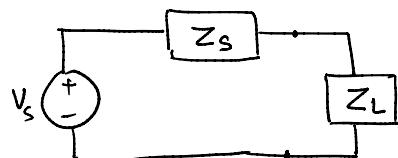

$$R_s = R_L$$

Max power delivered to load,
when $Z_L = Z_s^*$

Impedance Matching :-

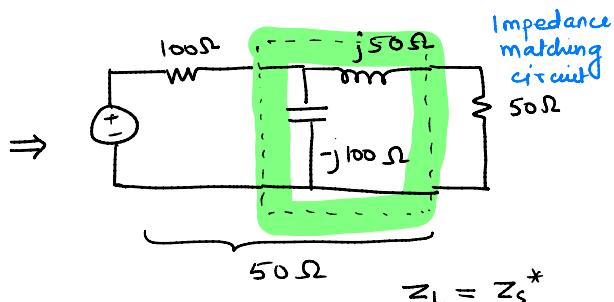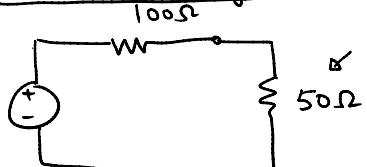

Effective value (RMS value) of voltage and current:-

$$v(t) \xrightarrow{i(t)} \frac{V_{\text{eff}}}{R} \xrightarrow{I_{\text{eff}}}$$

$$v(t) \leftarrow P_{\text{avg}} = P_{\text{avg}}$$

$$\Rightarrow \frac{1}{T} \int_0^T i^2(t) R dt = I_{\text{eff}}^2 R = \frac{V_{\text{eff}}^2}{R}$$

$$\Rightarrow I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \text{Root mean square}$$

Sinusoidally varying sources

$$i(t) = I_m \cos(\omega t + \phi)$$

$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t + \phi) dt}$$

$$I_{\text{eff}} = \frac{I_m}{\sqrt{2}}$$

$2 \cos^2 x = \cos 2x + 1$

$$T = \frac{2\pi}{\omega} = \frac{1}{f}$$

rms value

Suppose, $I = 10 \angle 90^\circ A$

$$\Rightarrow I = \underbrace{\frac{10}{\sqrt{2}}}_{\text{rms}} \angle 90^\circ A \text{ rms}$$

$$V_{\text{eff}} = \frac{V_m}{\sqrt{2}}$$

rms value

$$V_1 = 100 \angle -60^\circ V \text{ rms}$$

$$V_1 = 100\sqrt{2} \angle -60^\circ V$$

Apparent Power

$$P_{\text{apparent}} = I_{\text{eff}} V_{\text{eff}}$$

Power factor

$$\text{PF} = \frac{\text{average power}}{\text{apparent power}} = \frac{(V_m I_m / 2) \cos(\theta - \phi)}{V_{\text{eff}} I_{\text{eff}}} = \cos(\theta - \phi)$$

$$\text{PF} = \underbrace{\cos(\theta - \phi)}_{\text{Power factor angle}}$$

Review

Instantaneous Power : $p(t) = v(t) i(t)$

Average Power : $P_{avg} = \frac{V_m I_m}{2} \cos(\theta - \phi) = \frac{1}{2} \operatorname{Re}\{VI^*\}$

$$P_{avg, sources} = \sum P_{avg, elements}$$


P_{avg} for resistive load : $P_{avg} \neq 0$

P_{avg} for reactive load : $P_{avg} = 0$



$$Z = R + jX$$

↑ resistive
↓ reactive

Max. power transfer :

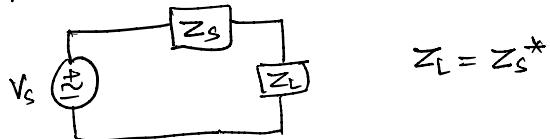

$$Z_L = Z_S^*$$

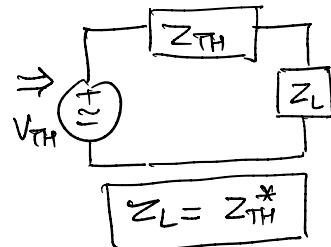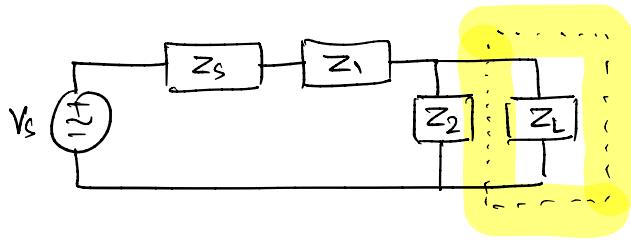

$$Z_L = Z_{TH}^*$$

Effective V and I values (RMS values)

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$i(t) = I_m \cos(\omega t + \phi)$$

$$I_{eff} = \frac{I_m}{\sqrt{2}}, \quad V_{eff} = \frac{V_m}{\sqrt{2}}$$

$$I = I_m \angle \phi = \sqrt{2} I_{eff} \angle \phi$$

Apparent Power

$$P_{apparent} = I_{eff} \cdot V_{eff}$$

$$\begin{array}{ll} I_{eff} & A_{rms} \\ V_{eff} & V_{rms} \\ \hline VA & (\text{volt-Ampere}) \end{array}$$

Power Factor

$$PF = \cos(\theta - \phi) = \frac{\text{Power}}{\text{Apparent}}$$

for purely resistive load: $PF = 1$ (max)

for purely reactive load: $PF = 0$ (min)

$$\begin{array}{ll} \theta - \phi & 90^\circ \\ \theta - \phi & -90^\circ \end{array}$$

Assume PF of a load = 0.5


$$\cos(\theta - \phi) = 0.5$$

$$\Rightarrow (\theta - \phi) = \pm 60^\circ$$

$PF = 0.5$ leading \rightarrow capacitive $(\theta - \phi) < 0$
 0.5 lagging \rightarrow inductive $(\theta - \phi) > 0$

I w.r.t. V

Example

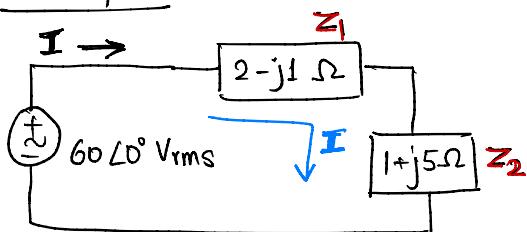


Find

- ① Average power delivered to each loads
- ② Average power supplied by source
- ③ Apparent power supplied by source
- ④ PF of combined load.

$$\text{① } P_{\text{avg}, z_1} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = \frac{1}{2} \text{Re}\{VI^*\}$$

$$= I_{\text{eff}}^2 R$$

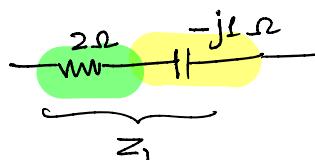

$$I =$$

Writing KVL:

$$- 60\angle 0^\circ V_{\text{rms}} + I (2 - j1 + 1 + j5) = 0$$

$$\Rightarrow I = \frac{60\angle 0^\circ V_{\text{rms}}}{3 + j4 \Omega} = \underbrace{12}_{I_{\text{eff}}} \angle -53.13^\circ A_{\text{rms}}$$

$$P_{\text{avg}, z_1} = (12)^2 2 = 288 \text{ W}$$

$$I = 12 \angle -53^\circ \text{ A rms}$$

$$i(t) = \frac{12}{I_{\text{eff}}} \cos(\omega t - 53^\circ) \text{ A rms}$$

I_{eff} (A rms) versus I_m (A)

$$I_{\text{eff}} = \frac{I_m}{\sqrt{2}} \Rightarrow I_m = I_{\text{eff}} \sqrt{2}$$


$$I_{\text{eff}} = 12$$

$$I_m = I_{\text{eff}} \sqrt{2} = \frac{12\sqrt{2}}{1}$$

$$i(t) = \frac{12\sqrt{2}}{I_m} \cos(\omega t - 53^\circ) \text{ A}$$

$$P_{\text{avg}} = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{\text{eff}} I_{\text{eff}} \cos(\theta - \phi)$$
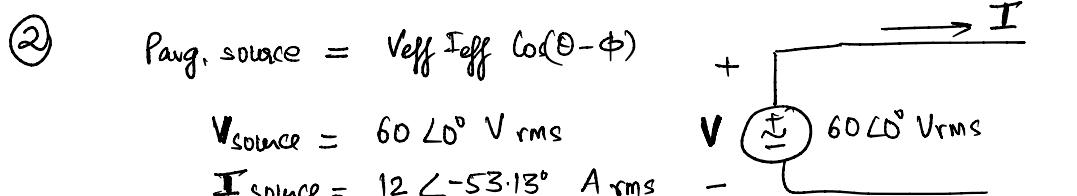
$$P_{\text{avg}, z_2} = I_{\text{eff}}^2 R = (12)^2 1 = 144 \text{ W}$$



$$P_{\text{avg, source}} = (60)(12) \cos(0 - (-53.13^\circ)) = 432 \text{ W}$$

$$P_{\text{avg}, z_1} = 288 \text{ W}, \quad P_{\text{avg}, z_2} = 144 \text{ W}$$

$$P_{\text{avg}, z_1} + P_{\text{avg}, z_2} = 432 \text{ W}$$

③ $P_{\text{apparent, source}} = I_{\text{eff}} V_{\text{eff}} = (60)(12) = 720 \text{ VA}$


④ PF of combined loads = PF of source

$$\text{PF} = \cos(\theta - \phi) = \cos(\theta + 53.13^\circ) = 0.6 \text{ lagging}$$

$(\theta - \phi) > 0 \rightarrow \text{lagging}$

$(\theta - \phi) < 0 \rightarrow \text{leading}$

$$P_{avg,z_1} = I_{eff}^2 R$$

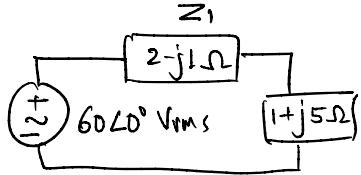

$$P_{avg,z_1} = V_{eff} I_{eff} \cos(\theta - \phi)$$

$$V_{Z_1} = 60 \angle 0^\circ \text{ Vrms} \times \frac{2 - j1}{3 + j4}$$

$$= 26.83 \angle -79.7^\circ \text{ Vrms}$$

$$I_{z_1} = I = 12 \angle -53.13^\circ \text{ Arms}$$

$$P_{\text{avg}, Z_1} = 26.83 \times 12 \times \cos(-79.7^\circ - (-53.13^\circ)) = 288 \text{ W}$$

$$\text{Power} = \frac{1}{2} \operatorname{Re} \{ \mathbf{V} \mathbf{I}^* \} ; \quad \mathbf{V} = V_m \angle \theta \\ \mathbf{I} = I_m \angle \phi$$

$$V_{eff} = V_{eff} \angle \theta = \frac{V_m}{\sqrt{2}} \angle \theta$$

$$I_{eff} = I_{eff} \angle \phi = \frac{Im}{\sqrt{2}} \phi$$

$$P_{\text{average}} = \operatorname{Re} \left\{ \mathbf{V}_{\text{eff}}^* \mathbf{I}_{\text{eff}} \right\}$$

Complex Power

$$S = V_{\text{eff}} I_{\text{eff}}^*$$

 { Not a phasor of power.
This is a complex number.

$$S = (V_{eff} \angle \theta^\circ) (I_{eff} \angle -\phi) = V_{eff} \cdot I_{eff} e^{j(\theta-\phi)}$$

$$S = P + jQ$$

$$|S| = V_{\text{eff}} I_{\text{eff}} = \text{Papparent (VA)}$$

$$Z = R + jX$$

Purely resistive load $Z = R, X = 0$

$$S = P + jQ \rightarrow V_{\text{eff}} I_{\text{eff}} \frac{\sin(\theta - \phi)}{0}$$

\downarrow
 $V_{\text{eff}} I_{\text{eff}} \cos(\theta - \phi)$

$$P \neq 0$$

$$Q = 0$$

Purely reactive load $Z = jX, R = 0$


$$S = P + jQ$$

$$P = 0$$

$$Q \neq 0$$

Q signifies energy flow rate into or out of reactive component of load.

Example

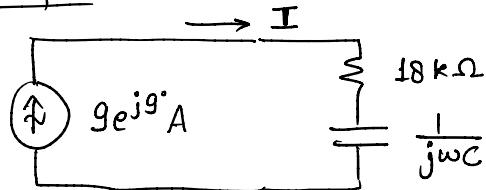

Assume $C = 1 \mu F, \omega = 45 \text{ rad/s}$

Find:

- (1) Complex power provided by source
- (2) Time-average power absorbed by combined load.

Find

- (3) Reactive power absorbed by combined load
- (4) Apparent power absorbed by " "
- (5) Power factor of " "

$$S = 1.158 \times 10^6 \angle -50.99^\circ \text{ VA}$$

$$P_{\text{avg}} = 7.29 \times 10^5 \text{ W}$$

$$Q = -9 \times 10^5 \text{ VAR}$$

$$|S| = P_{\text{apparent}} = 1.158 \times 10^6 \text{ VA}$$

$$\text{PF} = 0.629 \text{ leading}$$


$$p(t) = 7.29 \times 10^5 + 1.158 \times 10^6 \cos(90t - 33^\circ) \text{ W}$$

Module 4

Polyphase Circuits

(Chapter 12 of textbook)

Three-phase source

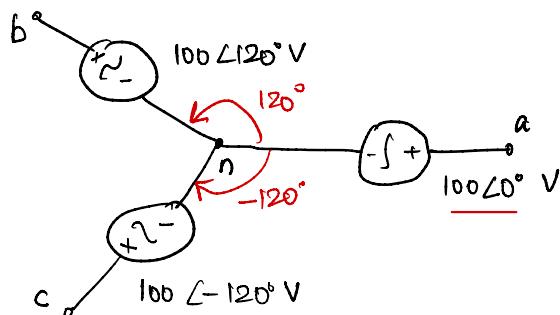

$$V_{an} = 100\angle 0^\circ \text{ V}$$

$$V_{bn} = 100\angle 120^\circ \text{ V}$$

$$V_{cn} = 100\angle -120^\circ \text{ V}$$

$$\left. \begin{aligned} |V_{an}| &= |V_{bn}| = |V_{cn}| \\ \rightarrow V_{an} + V_{bn} + V_{cn} &= 0 \end{aligned} \right\} \text{Balanced Source}$$

Freq. Domain

$$100\angle 0^\circ$$

$$100\angle 120^\circ$$


$$100\angle -120^\circ$$

Time Domain

$$100 \cos(\omega t)$$


$$100 \cos(\omega t + 120^\circ)$$

$$100 \cos(\omega t - 120^\circ)$$

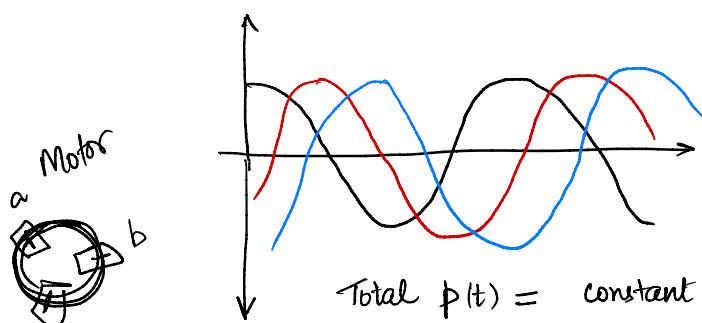

Total $p(t) = \text{constant}$ for three-phase sources
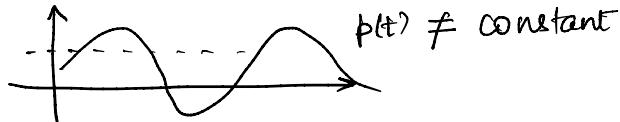
$$\text{for single phase source: } p(t) = \frac{1}{2} V_m I_m \cos(\theta - \phi) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta - \phi)$$




Advantages of three-phase sources are


- constant power and constant torque to large motors.
- more economical since motors are more efficient.

$\theta^\circ, \theta - 180^\circ$

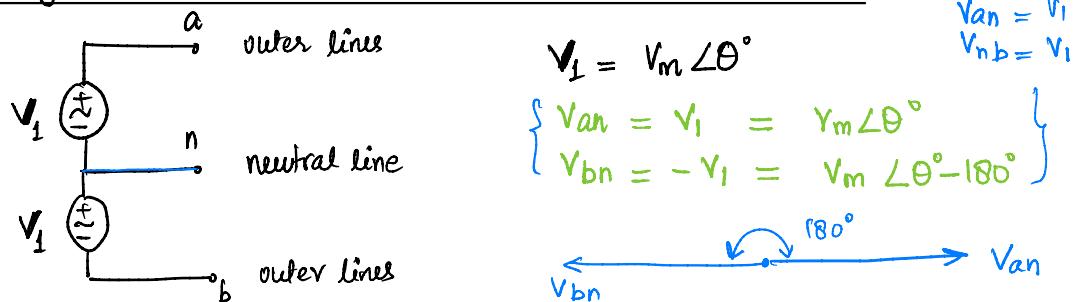Single-Phase Three-Wire Source (Two-phase source)



Double Script Notations:

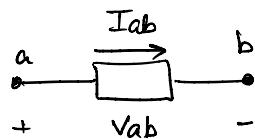

V_{an} = voltage at point a w.r.t. voltage at point n


$$V_{ab} = V_{an} - V_{bn} = V_{an} + V_{nb}$$

$$V_{bn} = -V_{nb}$$

I_{ab} = current flowing from point a to point b.

Balanced Single-Phase Three-Wire Source:


$$\left. \begin{array}{l} |V_{an}| = |V_{bn}| \\ V_{an} + V_{bn} = 0 \end{array} \right\} \text{Balanced source}$$

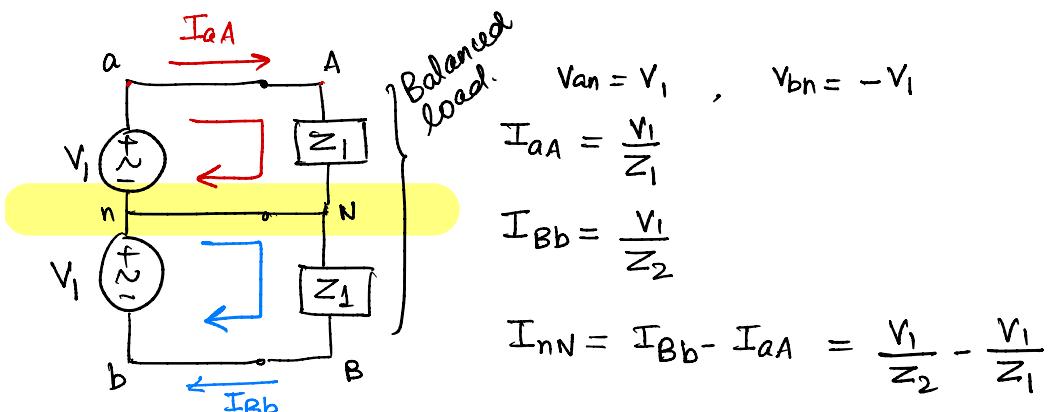

Assume $Z_1 = Z_2$ (Balanced load)

$$I_{nN} = \frac{V_1}{Z_1} - \frac{V_1}{Z_1} = 0$$

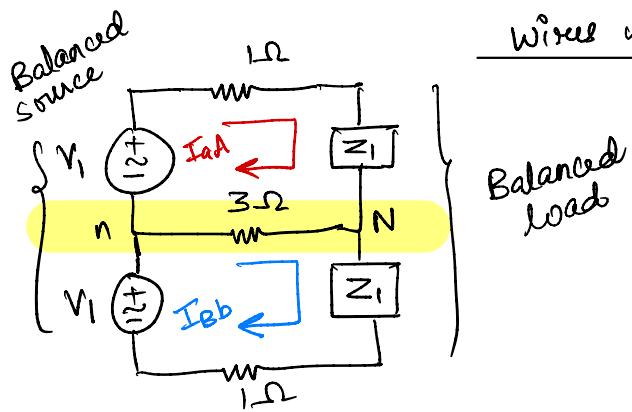
For balanced source } current in neutral line $I_{nN} = 0$
and balanced load }



Wires with non-zero resistance

$$I_{BN} = 0 = I_{Bb} - I_{aA}$$

Example

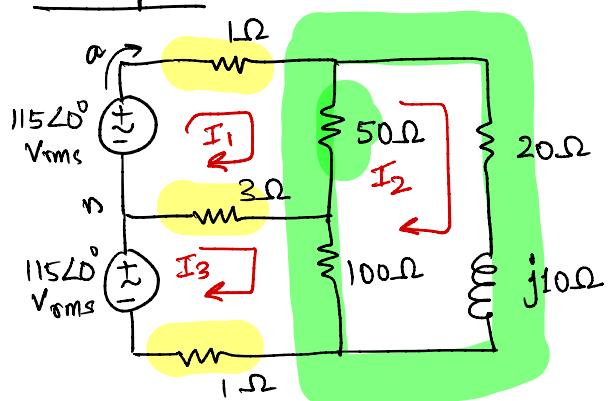

Find

- ① Average power delivered to each of three loads
- ② Avg power lost in outerlines and neutral line.
- ③ Avg power provided by source.

Line resistances

loads

Using mesh analysis

$$-115\angle 0^\circ + 1(I_1) + 50(I_1 - I_2) + 3(I_1 - I_3) = 0$$

$$50(I_2 - I_1) + (20 + j10)I_2 + 100(I_2 - I_3) = 0$$

$$-115\angle 0^\circ + (I_3 - I_1)3 + (I_3 - I_2)100 + I_3(1) = 0$$

$$\rightarrow I_1 = 11.24 \angle -19.83^\circ \text{ Arms}$$

$$I_2 = 9.389 \angle -24.47^\circ \text{ Arms}$$

$$I_3 = 10.37 \angle -21.80^\circ \text{ Arms}$$

$$I_1 - I_2 = 11.24 - 9.389$$

Avg power delivered to loads:

$$P_{avg, 50\Omega} = |I_2 - I_1|^2 (50) \\ = 206 \text{ W}$$

$$P_{avg, 100\Omega} = 117 \text{ W}$$

$$P_{avg, 20+j10\Omega} = I_2^2 (20) = 1763 \text{ W}$$

$$\text{Total power delivered to loads} = 2086 \text{ W}$$

Avg power lost in lines

$$P_{avg, aa} = |I_1|^2 1 = 126 \text{ W}$$

$$P_{avg, bb} = |I_3|^2 1 = 108 \text{ W}$$

$$P_{avg, nn} = |I_3 - I_1|^2 3 = 3 \text{ W}$$

$$\text{Total power lost in lines} = 237 \text{ W}$$

Power supplied by sources

$$P_{avg, an} = V_{an} I_{na} \cos(\theta - \phi) \\ = 115 \times 11.24 \cos(0 - (-19.83^\circ)) \\ = 1216 \text{ W}$$

$$V_{an} = 115 \angle 0^\circ \text{ V}_{rms}$$

$$I_{na} = I_1$$

$$P_{avg, nb} = 115 \times 10.37 \cos(21.80^\circ) \\ = 1107 \text{ W}$$

$$\text{Total power supplied} = 2323 \text{ W}$$

$$P_{supplied} = P_{delivered} + P_{loss}$$

① Example : Consider $V_{12} = 9 \angle 30^\circ$, $V_{32} = 3 \angle 130^\circ$
 find $V_{21} = 9 \angle -150^\circ$, $V_{13} = V_{12} + V_{23}$

② Consider a single-phase three-wire balanced source connected to a balanced load. $f = 50 \text{ Hz}$, $V_{an} = 115 \angle 0^\circ \text{ V}$

- Find power factor of the load if capacitor is omitted.
- find value of C that will lead to a unity power factor of total load.

